

Q1) a-Using RTD PT100 for temperature range (22C to 190C), design a signal conditioning circuit for (0-3V) ADC. (use voltage divider circuit, $V_s=9V$, $R_1=200\Omega$).

b-If we will send the sensor output for a distance with same voltage reference.

c-What is the ADC digital output if the temperature is 100C.

d-What is the temperature if the ADC output is (10011110).

$$V_{ref} = 2V \quad [14 \text{ pts}]$$

Q2) Using Acceleration sensor (sensitivity = 0.4mA/g), with offset $7 \text{mA}@0g$, for the range ($\pm 30g$) and using voltage to frequency converter VFC (scale factor = $4V/6 \text{KHz}$).

a-Draw the block diagram of the operation.

b-Calculate the sensor output range, and VFC output range, digital output of counter if the sampling is each 0.2Sec.

c-What is the value of the output of the counter if the acceleration is $-0.5g$.


[10 pts]

Q3) Barometer sensor sensitivity is 5mV/bar , and $5\Omega/\text{cm}$ pot. level sensor for 150cm range used for measuring level ($V_s=9V$ use, $R_1=150\Omega$). Design circuit to turn ON green LED if (level more than 70cm and pressure less than 5bar), red LED if one of them opposite these values.

[10 pts]

Q4) What is the value of voltmeters and ADC and DAC outputs.

[8 pts]

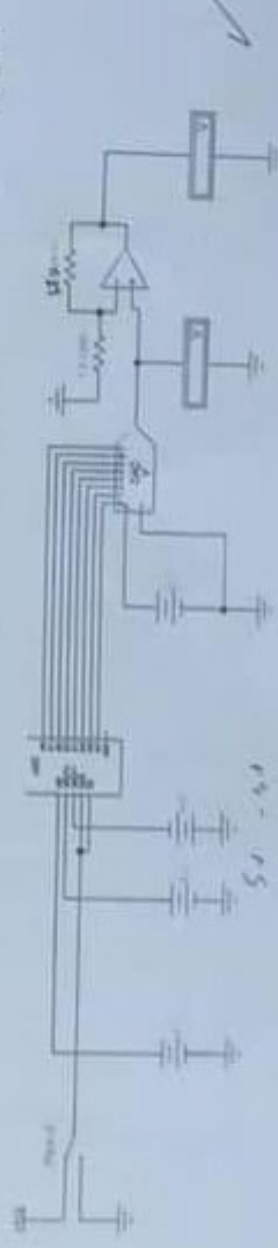

Q5) a- Using Thermocouple sensor Type K with $0C$ reference, What is the value of temperature if its output is 19mV , What is its output at the temperature $V_{K10}(-40C)=?$. [8pts]

Q1.a) A liquid level sensor has an input range of 0 to 15cm. Use the calibration results given in the table to estimate the maximum hysteresis as a percentage of f.s.d.

Liquid h cm	0	1.5	3	4.5	6	7.5	9	10.5	12	13.5	15
Output volts h increasing	0	0.35	1.42	2.4	3.43	4.35	5.61	6.5	7.77	8.88	10.2
Output volts h decreasing	0.14	1.25	2.32	3.45	4.43	5.7	6.78	7.8	8.87	9.65	10.2

Q1.b) A temperature sensor has a span of 20.250C. A measurement results in a value of 55C for the temperature. Specify the error if the accuracy is:

1- $\pm 0.5\%$ fs 2- $\pm 0.75\%$ of span 3- $\pm 0.8\%$ of reading

What is the possible temperature in each case?

[6 pts]

Q2.a) Drive the equation of the bridge offset voltage for the current balance bridge?

Q2.b) Design a high-pass RC filter that must drive 120Hz noise down to 1% using a capacitor 0.01 μ F. Specify the attenuation of a 30KHz signal?

Q2.c) Signal conditioning analysis shows that the following equation must relate output voltage to input voltage: $V_o = 3.35V_{in} + 2.68$

Design circuits to do this using (a) a summing amplifier (b) a differential amplifier?

[8 pts]

Q3.a) A 12-bit bipolar DAC has a 10V reference

1- What output voltage results from digital input of 4A6 H.

2- An output of 4.74V is needed. What digital input would come closest to this value? By what percentage is the actual output different?

Q3.b) Using timing diagram, explain the control lines that coordinate the operation of ADCs?

[6 pts]

Good Luck

$$V_o = \frac{R_f}{R_n} \sqrt{V_{in}} - \frac{R_f \sqrt{V_{in}}}{R_n}$$

$$\frac{R_f}{R_n} = 1$$

EE463

Q1) Temperature sensor sensitivity is $4\Omega/^\circ\text{C}$, in the range $(\pm 25^\circ\text{C})$ and its value at 0°C is 280Ω . Using Wheatstone bridge convert its range to volt, and send its value using $(4\text{mA} \rightarrow 20\text{mA transmitter})$ and prepare it for 8bit ADC with voltage reference $0-5\text{V}_{\text{ref}}$.

a) What is the digital output of ADC at the temperature -2°C . [12 pts] (33)d

Q2) Accelerometer sensor sensitivity is 0.33mA/g used for measuring Acceleration in the range $(\pm 20\text{g})$. Design signal condition circuits for bipolar (8 bit) ADC with voltage reference $\pm 4\text{V}$.

a) What is the digital output of ADC at the acceleration is -3g .

b) What is the acceleration when the digital output is 06H. -19 -06 (42.8%)

Q3) Design the signal conditioning circuits to connect the sensor to 10 bit ADC with voltage reference $(0-5\text{V})$, where: sensor output range $(-150 \sim +150\text{mV})$ with frequency 15Hz . Noise signal 20mV with frequency 150Hz , and design filter that Attenuate the noise signal to 25% , and taking in account the effect of the filter on the sensor signal.

[10 pts]

Q4) Using Thermocouple sensor Type J with 0°C reference, find the value of its output at 32°C . Design circuit to operate cooler if the temperature is more than 32°C , and using RTD with the following table using linear approximation of resistance versus temperature find the value of the RTD at 13°C and design circuit operate heater if the temperature is less than 13°C .

[12 pts]

Temperature ($^\circ\text{C}$)	0	5	10	15	20
Resistance (Ω)	107.6	109.1	110.2	111.1	111.7

Q5) What is the sampling and sample and hold and aliasing and oversampling (Draw as you can). [4 pts]

Q1.a) An alarm light goes ON when a pressure sensor voltage rises above 4.00 V. The pressure sensor outputs 20 mV/kPa and has a time constant of 4.9 s. How long after the pressure rises suddenly from 100 kPa to 400 kPa does the light go ON?

Q1.b) A load cell is calibrated at $21\epsilon^{\theta}$ and has the following deflection/load characteristic:

Load(kg)	0	50	100	150	200
Deflection (mm)	0	1	2	3	4

When used at $35\epsilon^{\theta}$, its characteristic changes to the following:

Load(kg)	0	50	100	150	200
Deflection (mm)	0.2	1.3	2.4	3.5	4.6

Determine the sensitivity coefficients

(10 pts)

Q2.a) A measurement signal has a frequency less than 1KHz, but there is unwanted noise at about 1MHz. Design a filter that attenuate the noise to 1% using a capacitor $0.01\mu\text{f}$. What is the effect on the measurement signal at its maximum of 1KHz (give a comment on the result)?

Q2.b) Signal conditioning analysis shows that the following equation must relate output voltage to input voltage: $V_o = 3.35V_{in} - 2.68$. Design circuits to do this using a differential amplifier?


(12 pts)

Q3.a) Using timing diagram, explain the control lines that coordinate the operation of ADCs?

Q3.b) Design a 5-bit weighted-resistor DAC whose full-scale output voltage is -15v. Logic levels are 1=5v and 0=0v. What is the output voltage when the input is 01010?

(10 pts)

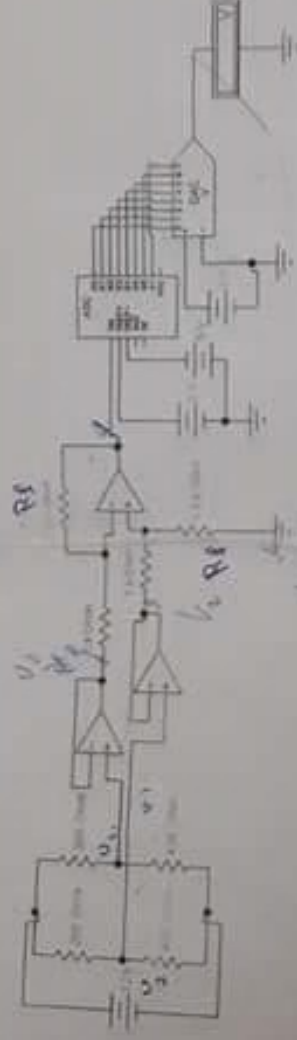Q1) From the circuit below what is the value of ADC digital outputs and DAC analog output.



Q2) A measurement signal has a frequency 800Hz, but there is unwanted noise at about 10KHz. Design filter that attenuate noise as possible with better effect on the signal(give the 3 attempts with comments).

Q3) using accelerometer which sensitivity 0.3mA/g , and using $R=200\Omega$ for voltage conversion, and using VFC which scale factor 5KHz/V , sampling time 0.1sec :

- Draw the block diagram of the operation
- What is the digital output (in binary) if the acceleration is 11 g .
- What is the value of acceleration if the digital output is $(190)_{10}$.

Good Luck (Zeyad Hamza)

$$T = \frac{V_{SD}}{V_{SD}}$$

Q1) a- Using RTD PT100 for temperature range (22°C to 190°C), design a signal conditioning circuit for (0-3V) ADC. (use voltage divider circuit, $V_S=9V$, $R1=200\Omega$).

~~b- If we will send the sensor output for a distance with same voltage reference.~~

c- What is the ADC digital output if the temperature is 100°C.

d- What is the temperature if the ADC output is (10011110).

[14 pts]

Q2) Using Acceleration sensor (sensitivity $-0.14mV/g$), with offset $7mA @ 0g$, for the range ($\pm 30g$) and using voltage to frequency converter VFC (scale factor $= 4V/6KHz$).

a- Draw the block diagram of the operation.

b- Calculate the sensor output range, and VFC output range, digital output of counter if the sampling is each 0.2Sec.

c- What is the value of the output of the counter if the acceleration is -0.5g.


[10 pts]

Q3) Barometer sensor sensitivity is $5mV/bar$, and $5\Omega/cm$ pot. level sensor for 150cm range used for measuring level ($V_S=9V$ use, $R1=150\Omega$). Design circuit to turn ON green LED if (level more than 70cm and pressure less than 5bar), red LED if one of them opposite these values.

[10 pts]

Q4) What is the value of voltmeters and ADC and DAC outputs.

[8 pts]

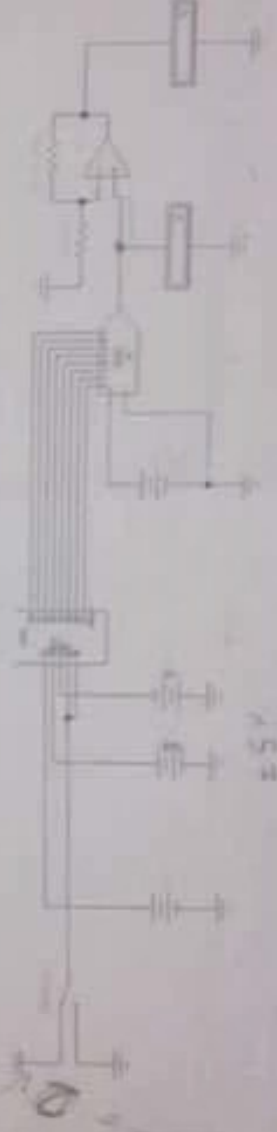

Q5) a- Using Thermocouple sensor Type K with 0°C reference, What is the value of temperature if its output is 19mV, What is its output at the temperature $V_{K10}(-40°C)=7$. [8pts]

Q1) From the circuit below what is the value of ADC digital outputs and DAC analog output.

Q2) A measurement signal has a frequency 800Hz, but there is unwanted noise at about 10KHz. Design filter that attenuate noise as possible with better effect on the signal(give the 3 attempts with comments.)

Q3) using accelerometer which sensitivity 0.3mA/g , and using $R=200\Omega$ for voltage conversion, and using VFC which scale factor 5KHz/V , sampling time 0.1sec .

- Draw the block diagram of the operation
- What is the digital output(in binary) if the acceleration is 11 g.
- What is the value of acceleration if the digital output is (190)₁₀

Q1) What elements of data acquisition system, explain two of them

Q2) Temperature sensor which sensitivity = $0.11 \text{ mA}/^\circ\text{C}$, and its value @ $0^\circ\text{C} = 5 \text{ mA}$, for temperature range ($\pm 40^\circ\text{C}$), and using $R = 150 \Omega$ for converting to volt, voltage supply 12 V .

A- Design circuit to send the sensor output for long distance and for ADC ($V_{\text{ref}} = 0-4 \text{ V}$).

B- What is the digital output of ADC if the temperature is 33°C , -14°C ?

C- What is the temperature if the digital output is 88H?

Q3) Sensor used to measure pressure in range ($0-30 \text{ bar}$) with sensitivity ($7 \text{ mV}/\text{bar}$), RTD PT100 to measure temperature, potentiometer used to measure the level as shown in figure.

A- Design circuit to turn ON buzzer if (temp is more than 49°C or pressure is more than 10 bar or level is less than 33 cm)

B- Turn ON release valve if pressure is more than 15 bar .



EE463 Final Exam- Time: 2 hr Spring 2019 25/9/2019

- Q1) a-What is the meaning of single ended signal, differential signal and give example. [6 pts]
b- What is sample and what is hold and when we use them. [6 pts]

Q2) Using Temperature sensor (RTD-PT100), in the range (30C to 90C) and using Wheatstone bridge ($V_s=9V$, $R_1=110$, $R_2=120$), and using voltage to frequency converter VFC (scale factor = $10\text{KHz}/(1.12V)$).

- a- Calculate the sensor output range, Wheatstone bridge output range and VFC output range.
b- Using a counter to convert to digital with sampling rate 180 sample/Sec, What is the output range of the counter, what is the value of the output of the counter if the temperature is 100C. 552
c- Draw Block diagram of the circuit. [16 pts]

Q3) An accelerometer sensor sensitivity is 0.145mA/g , used for measuring pressure in the range ($\pm 20\text{ g}$), and the value of its output @ 0 g is 5.2mA , using 190Ω converting to volt resistance, Design signal condition circuits for bipolar (8 bit) ADC with voltage reference $\pm 4V$.

- a) Calculate sensor output range (current, voltage, Binary).
b) What is the digital output of ADC at the acceleration is 8 g .
c) What is the value of acceleration when the digital output is 0DH.92H. [15 pts]
d) If the frequency of the signal is 120Hz and there is unwanted noise with frequency 15KHz , design filter that attenuate the noise to 18% of its value, calculate the effect on the sensor output range. [05 pts]

Q4) Using RTD with the following table using Quadratic approximation of resistance versus temperature find the value of the RTD at 12.4°C .

Temperature ($^\circ\text{C}$)	0	5	10	15	20
Resistance (Ω)	103.6	105.1	106.5	107.1	108.3

[08 pts]

Good Luck (Zeyad)

D) (16011110) = 158 $V_o = D_o \Delta = 1.8515625V$

$V_{in} = \frac{V_o \times 10^6}{R} = 3.797362007V$

$RTD = \frac{V_o R}{V_s - V_o} = 145.9783291\Omega$

$T = \frac{RTD - 100}{0.39} = 117.8931516^\circ C$

b) we use (4-20) mA transmitter where its Voltage range in (1-5)V and the output from the Voltage Divider circuit is suitable and in range of use.

Q20 Acceleration $S = 0.14mA/g$ @ $D_g = 7mA \pm 30g$

Use VFC (4V/5 kHz) = 1.5 kHz



$T_{0.02}$

b) Range (-30g to +30g)

$(7mA \pm 0.19330 \pm 2.8mA) \quad 7 \pm 0.14 \times 30 = 11.2mA$

assume $R = 100\Omega$

$V_o = IR \Rightarrow (0.28 \sim 1.12)V$

output from VFC = $(0.28 \times 1.5) \quad 1.12 \times 1.5$


$= (420Hz) \quad 1680Hz$

(1680×0.2)

336

Coater output range = $((420 \times 0.2) \quad (1680 \times 0.2))$

$(84 \quad 336)$

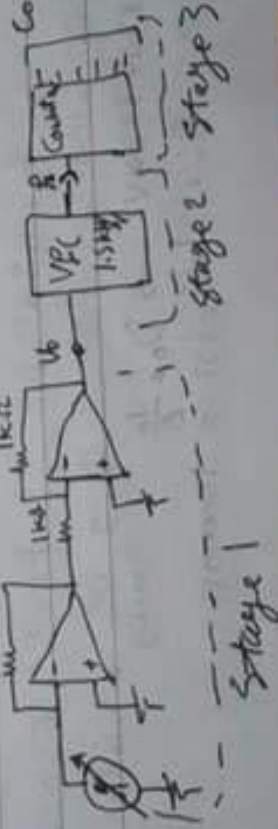

Spring 2018

Q1: Single ended Signal is a Constant output Signal depends on the Parameters of the Circuit & differential Signal is a Difference Signal at the output between two terminals of a Bridge.

We use Sample and hold because ADC needs a finite amount of time to measure the Signal Voltage.

Q2: 5 mV/K , $(30-120)^\circ\text{C}$ V_{PC} 0.5 kHz/V f_s 10 Hz
 T_s 0.1 s

Voltage range $(30 \times 5 \text{ mV/K} = 150 \text{ mV})$ $120 \times 5 \text{ mV/K} = 600 \text{ mV}$
 Frequency range $(150 \times 0.5 = 75 \text{ Hz})$ $600 \times 0.5 = 300 \text{ Hz}$
 Counter range $(75 \times 0.1 = 7.5 = 7)$ $300 \times 0.1 = 30$

For Temperature 112°C $V_o = 112 \times 5 \text{ mV/K} = 560 \text{ mV}$
 $V_{PC} = 0.5 \times 560 = 280 \text{ Hz}$, $C_o = 280 \times 0.1 = 28$ ✗

Q3: 0.13 mA/bar range $\pm 20 \text{ bar}$ @ $0 \text{ bar} = 0 \text{ mV}$ $R = 150$

Using bipolar ADC $8 \text{ bit} \pm 4 \text{ V}$

Amperage range $(-20 \times 0.13) \text{ mA} = -2.6 \text{ mA}$ $\sim (20 \times 0.13) \text{ mA} = 2.6 \text{ mA}$

Voltage range $(1.4 \times 150 = 210 \text{ mV}) \sim 6.6 \times 150 = 990 \text{ mV}$

$-4 = 0.210 \text{ M} + \text{offset}$ $M = \frac{400}{39}$ $V_o = M V_{in} + \text{offset}$

$+4 = 0.99 \text{ M} + \text{offset}$ $\text{offset} = -\frac{80}{13}$ $D = \frac{8}{2^6} = \frac{1}{32}$

a) in 8 bar find $D_o \Rightarrow ((8 \times 0.13) + 4) \times 150 = 756 \text{ mV}$

$V_o = \frac{400}{39} \times 0.756 - \frac{80}{13} = 1.6$

$D_o = \frac{1.6 \times 128 + 28}{256} = 0.55$ ✗
 Δ $9.6 \times 32 = 179.2 \times 179 = (10110011)_2$ ✗

Q1) What elements of data acquisition system, explain two of them

Q2) Temperature sensor which sensitivity = $0.11 \text{ mA}/^\circ\text{C}$, and its value @ $0^\circ\text{C} = 5 \text{ mA}$ for temperature range ($\pm 40^\circ\text{C}$), and using $R = 150 \Omega$ for converting to volt, voltage supply 12 V .

A- Design circuit to send the sensor output for long distance and for ADC (V_{ref} $0 \sim 4 \text{ V}$).


B- What is the digital output of ADC if the temperature is 33°C , -14°C ?

C- What is the temperature if the digital output is 88 H ?

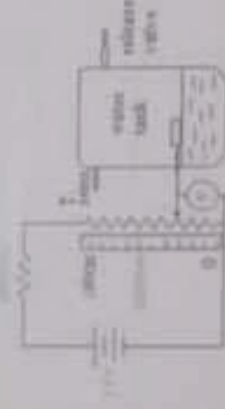Q3) Sensor used to measure pressure in range ($0 \sim 30 \text{ bar}$) with sensitivity ($7 \text{ mV}/\text{bar}$), RTD PT100 to measure temperature, potentiometer used to measure the level as shown in figure.

A- Design circuit to turn ON buzzer if (temp is more than 49°C or pressure is more than 10 bar or level is less than 33 cm)

B- Turn ON release valve if pressure is more than 15 bar .



Q1) What elements of data acquisition system, explain two of them

Q2) Temperature sensor which sensitivity = $0.1 \text{ mA}/^\circ\text{C}$, and its value @ $0^\circ\text{C} = 5 \text{ mA}$, for temperature range ($\pm 40^\circ\text{C}$), and using $R = 150 \Omega$ for converting to volt, voltage supply 12V.

A- Design circuit to send the sensor output for long distance and for ADC ($V_{\text{ref}} = 0-4 \text{ V}$).


B- What is the digital output of ADC if the temperature is 33°C , -14°C ?

C- What is the temperature if the digital output is 88H?

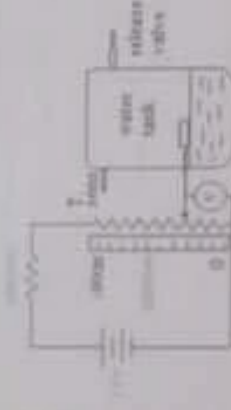Q3) Sensor used to measure pressure in range ($0-30 \text{ bar}$) with sensitivity ($7 \text{ mV}/\text{bar}$), RTD PT100 to measure temperature, potentiometer used to measure the level as shown in figure.

A- Design circuit to turn ON buzzer if (temp is more than 49°C or pressure is more than 10 bar or level is less than 33cm)

B- Turn ON release valve if pressure is more than 15 bar.



27/12/2016

University of Tripoli - Faculty of Engineering		20/12/2016	
Electrical & Electronic Engineering Department			
2nd Exam	Time: 1.30 hr	Fall 2016	

EE463

Q1.a) An ADC that will encode pressure data is required. The input signal is 666.6 mV/psi.
a. If a resolution of 0.5 psi is required, find the number of bits necessary for the ADC. The reference is 10.0 V?

b. Find the maximum measurable pressure?

Q1.b) An 8-bit DAC with a 5.00-V reference connects to a light source with an intensity given by $I_s = 4.5 \times 10^{-6} \text{ W/m}^2$. What intensities are produced by digital inputs of 1BH, 7AH? [8 pts]

Q2.a) Describe the working principle of thermocouple sensors. What are techniques employed for reference junction compensation?

Q2.b) An RTD has $\alpha = 0.005/^\circ\text{C}$, $R = 500\Omega$, and a dissipation constant of $P_D = 30 \text{ mW/}^\circ\text{C}$ at 20°C . The RTD is used in a bridge circuit with $R_1 = R_2 = 500\Omega$ and R_3 a variable resistor used to null the bridge. If the supply is 10 V and the RTD is placed in a bath at 0°C , find the value of R_3 to null the bridge. [12 pts]

Q2.c) A resistive element of a wire-wound pot is made from 10in of $100\Omega/\text{in}$ resistance and is wound as a coil of 200 loops, the range of the pot is 350 degree. What is the resolution of this pot? [12 pts]

Q3.a) Describe the working principle of linear variable differential transformer?

Q3.b) A strain gauge has $GF = 2.06$ and $R = 120 \Omega$, and is made from wire with $\alpha = 0.0034/^\circ\text{C}$ at 25°C . The dissipation factor is given as $P_D = 25 \text{ mW/}^\circ\text{C}$. What is the maximum current that can be placed through the SG to keep self-heating errors below 1 micro of strain?

Q3.c) Water is pumped through a 1.5in diameter pipe with a flow velocity of 2.5ft/s. Find the volume flow rate and weight flow rate. The weight density is 62.4 lb/ft³? [12 pts]

ϕ

$$\phi = AV$$

Good Luck

Q1. If $g_m = 0.59$ find C_m
 $C_m = \left(\left[(8 \times 0.14) \cdot 7m \right] \times 0.1k\Omega \right) \times 1.5kH/V \Rightarrow T$

$C_m = 201.9 = 202 \text{ fF}$


Q2. $S = 5mV/mm$, $5.8\mu m$ pit for $150nm$
 Use $V_S = 9V$, $R_1 = 150\Omega$, on Green if more than $70nm$ and less $5nm$ red on it else

Q3. $5nm \Rightarrow 5 \times 5mV/mm = 25mV$

Q4. $70nm \Rightarrow 70 \times 5mV/mm = 350mV$

Q5. $150nm \Rightarrow 150 \times 5mV/mm = 750mV$

by using Comparator

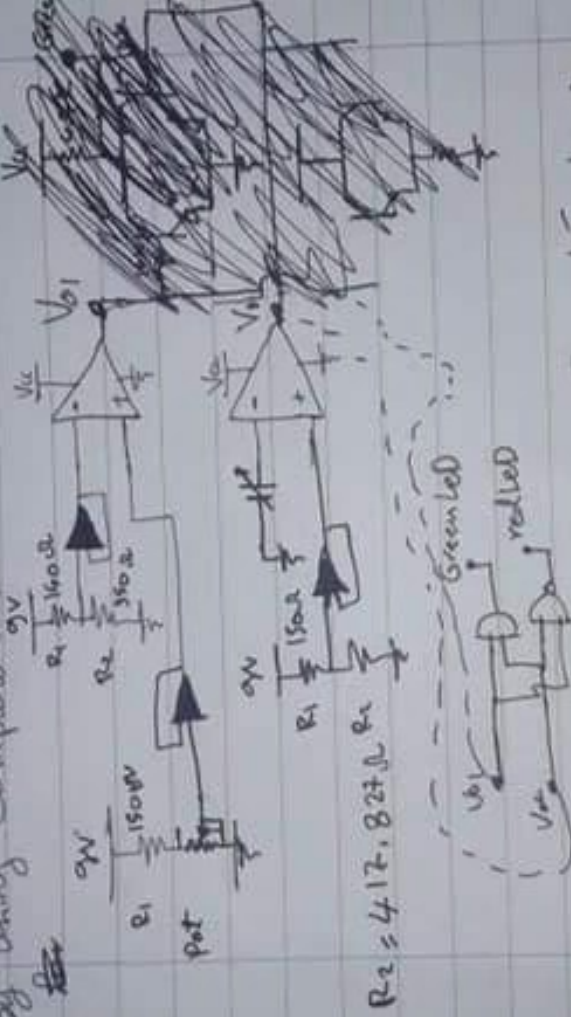

Q6. $R_2 = 417.82\Omega$

Q7. $R_1 = 150\Omega$

منش و افضة الهرة لكي سامه

تقريباً غير داخل من صطاني ج اول و مشر حالي

Superior Notepad

White/Blanc
Narrow Ruled/Règle étroite

12/2/2019

EL463

Q1) a-Using RTD PT100 for temperature range (22C to 190C), design a signal conditioning circuit for (0-3V) ADC. (use voltage divider circuit. $V_S=9V, R_1=200\Omega$).

b-If we will send the sensor output for a distance with same voltage reference.

c-What is the ADC digital output if the temperature is 100C.

d-What is the temperature if the ADC output is (10011110).

$$V_{CD} = 2V \quad [14 \text{ pts}]$$

Q2) Using Acceleration sensor (sensitivity -0.14 mA/g), with offset $7 \text{ mA}@0g$, for the range ($\pm 30g$) and using voltage to frequency converter VFC (scale factor $= 4V/6KHz$).


a-Draw the block diagram of the operation.

b-Calculate the sensor output range, and VFC output range, digital output of counter if the sampling is each 0.2Sec.

c-What is the value of the output of the counter if the acceleration is $-0.5g$. [10 pts]

Q3) Barometer sensor sensitivity is 5 mV/bar , and $5\Omega/\text{cm}$ pot. level sensor for 150 cm range used for measuring level ($V_S=9V$ use, $R_1=150\Omega$). Design circuit to turn ON green LED if (level more than 70 cm and pressure less than 5 bar), red LED if one of them opposite these values.

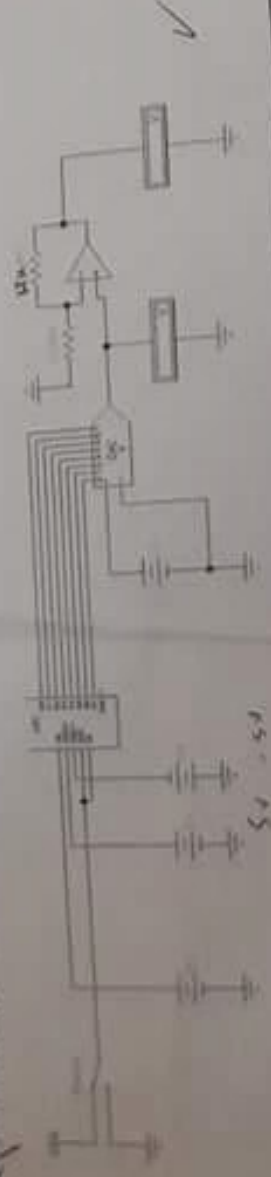Q4) What is the value of voltmeters and ADC and DAC outputs. [8 pts]



Q5) a- Using Thermocouple sensor Type K with $0C$ reference. What is the value of temperature if its output is 19 mV . What is its output at the temperature $V_{K10}(-40C)=?$. [8pts]

Good Luck (Zeyad)

5/20/12

Q3 b) $0.25 \times \frac{1}{\sqrt{1 + (\frac{150}{f_c})^2}} \Rightarrow f_c = \sqrt{\frac{150^2}{\frac{1}{0.25} - 1}} = \sqrt{\frac{150^2}{3}} = 10\sqrt{5} \approx 38.7298 \text{ Hz}$

the effect of filter on the signal ^{good}

$\frac{1}{\sqrt{1 + (\frac{150}{f_c})^2}} = \frac{0.25 \times 1}{\sqrt{1 + (\frac{150}{f_c})^2}}$ ~~Not the filter should be~~ ^{Very good signal}

Assume (HPF) $\Rightarrow f_c = \sqrt{\frac{f_1^2 - f_2^2}{f_1^2}} = \sqrt{\frac{140^2 - 0.25^2}{0.25^2}} \approx 580.947 \text{ Hz}$

(Effect of filter on the signal)


$\frac{f_1/f_c}{\sqrt{1 + (\frac{f_1}{f_c})^2}} \approx 2.58284 \times 10^{-4}$

Q4 a, b \rightarrow dis. ~~is~~

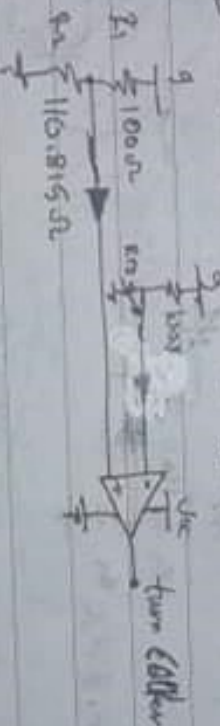c) RTD with linear Approximation find $R(13^\circ\text{C})$

$\alpha_o = \frac{1}{R_o} \left(\frac{R_o - R_i}{T_o - T_i} \right) = \frac{1}{110.2} \left(\frac{111.7 - 107.6}{20 - 0} \right) \approx \frac{41}{22040} \text{ } ^\circ\text{C}^{-1}$

$R_o R_o [1 + \alpha_o \Delta T] = 110.2 \left[1 + \frac{41}{22040} \times (15 - 0) \right] = 110.815$



Q5 from notebook

Q1) What elements of data acquisition system, explain two of them

Q2) Temperature sensor which sensitivity = $0.1 \text{ mA}/^\circ\text{C}$, and its value @ $0^\circ\text{C} = 5 \text{ mA}$, for temperature range ($\pm 40^\circ\text{C}$), and using $R = 150 \Omega$ for converting to volt, voltage supply 12V.

A- Design circuit to send the sensor output for long distance and for ADC (V_{ref} 0-4V).


B- What is the digital output of ADC if the temperature is 33°C , -14°C ?

C- What is the temperature if the digital output is 88H?

Q3) Sensor used to measure pressure in range (0-30 bar) with sensitivity ($7 \text{ mV}/\text{bar}$), RTD PT100 to measure temperature, potentiometer used to measure the level as shown in figure.

A- Design circuit to turn ON buzzer if (temp is more than 49°C or pressure is more than 10 bar or level is less than 33 cm)

B- Turn ON release valve if pressure is more than 15 bar.

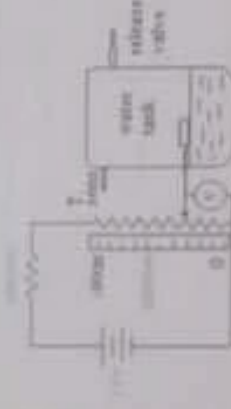

Spring 2017

Q1. 4.5V @ 220Ω Use Bridge and then 4-20mA and then 8bit ADC 0-5V



$$\text{rang } \pm 25\% \left((-25 \times 4) + 280 = 180\Omega \sim (25 \times 4) 280 = 380\Omega \right)$$

Using Bridge with the $R_1, R_2, R_3 = 180\Omega$

$$V_A = 9 \times \frac{180}{180+180} = 4.5V \quad V_B = 9 \times \frac{180}{180+180} = 4.5V$$

at nulling $V_{AS} = 0V$ ✗

$$\text{at maximum } V_0 = 9 \times \frac{380}{180+380} = 6.107142857V$$



$$V_{AB} = 1.607142857V \quad \text{rang } (0 \sim 1.607142857V)$$

Using Summing Circuit - to add the output of sensor with 1 output rang $(1 \sim 2.607142857V)$

We need SC for ADC

$$M = \frac{28}{9}$$
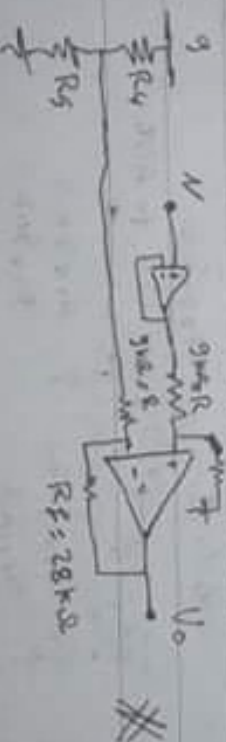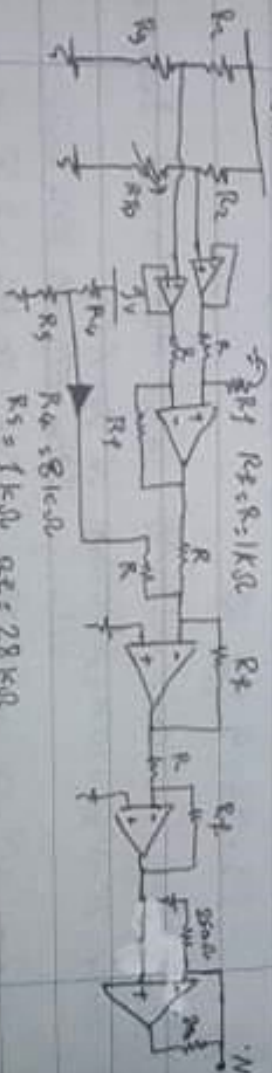
$$O = 6.1M + 0.85 \text{ at } 5 = 2.607142857M + 0.85 \text{ at offset } -\frac{28}{9} \quad V_0 = \frac{28}{9}(V_A - 1)$$



Supper Notepad

EE463

Q1) Temperature sensor sensitivity is $4\Omega/^\circ\text{C}$, in the range $(\pm 25^\circ\text{C})$ and its value at 0°C is 280Ω . Using Wheatstone bridge convert its range to volt, and send its value using (4mA $\pm 20\text{mA}$ transmitter) and prepare it for 8bit ADC with voltage reference $0-5\text{V}_{\text{ref}}$.
a) What is the digital output of ADC at the temperature -2°C . [12 pts] (33)d

Q2) Accelerometer sensor sensitivity is 0.33mA/g , used for measuring Acceleration in the range $(\pm 20\text{g})$. Design signal condition circuits for bipolar (8 bit) ADC with voltage reference $\pm 4\text{V}$. [10 pts] 103 or 106

a) What is the digital output of ADC at the acceleration is -3g .
b) What is the acceleration when the digital output is 06H. [19] 06(4E, 86s)

Q3) Design the signal conditioning circuits to connect the sensor to 10 bit ADC with voltage reference $(0-5\text{V})$, where: sensor output range $(-150 - +150\text{ mV})$ with frequency 15Hz . Noise signal 20mV with frequency 150Hz , and design filter that Attenuate the noise signal to 25% , and taking in account the effect of the filter on the sensor signal. [10 pts]

Q4) Using Thermocouple sensor Type J with 0°C reference, find the value of its output at 32°C . Design circuit to operate cooler if the temperature is more than 32°C , and using RTD with the following table using linear approximation of resistance versus temperature find the value of the RTD at 13°C and design circuit operate heater if the temperature is less than 13°C . [12 pts]

Temperature ($^\circ\text{C}$)	0	5	10	15	20
Resistance (Ω)	107.8	109.1	110.2	111.1	111.7

Q5) What is the sampling and sample and hold and aliasing and oversampling (Draw as you can). [4 pts]

Q1) Temperature sensor sensitivity is $0.42\text{mA}/^\circ\text{C}$, used for temperature range $(\pm 50^\circ\text{C})$.

Design signal condition circuits for bipolar (8 bit) ADC with voltage reference $\pm 3\text{V}$.


a) What is the digital output of ADC at the temperature 31°C , -20°C .

b) What is the temperature when the digital output is B6H. [10 pts]

Q2) Design the signal conditioning circuits to connect the sensor to 8 bit ADC with voltage reference $(0-10\text{V})$, where: sensor output range $(-100 \sim +100\text{ mV})$ with frequency 25Hz . Noise signal 20mV with frequency 260Hz , and using filter that Attenuate the noise signal to 29% of its value, and taking in account the effect of the filter on the sensor signal. [10 pts]

Q3) Using pressure sensor which sensitivity is $2.3\text{mV}/\text{bar}$, and temperature sensor which sensitivity is $10\mu\text{V}/^\circ\text{C}$ and its value at zero $^\circ\text{C} = 300\text{mV}$. Design circuit which open Valve when the pressure is more than 15bar , and operate heater when temperature is less than 20°C , and operate Red LED when both of them are ON. [10 pts]

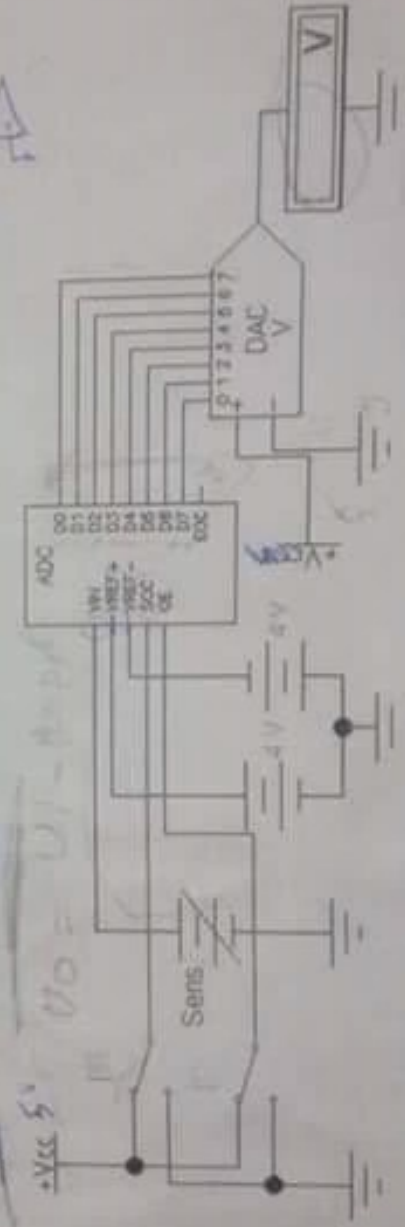Q4) What is the digital value of the ADC output and what is the analog value of DAC output at the temperature 23°C and -30°C . Where: sensor sensitivity $= 15\text{mV}/^\circ\text{C}$, sensor output at $0^\circ\text{C} = 100\text{mV}$, sensor range $\pm 50^\circ\text{C}$. [10 pts]



2664 32 168421

University of Tripoli - Faculty of Engineering
Electrical & Electronic Engineering Department

EE463 Final Exam Time: 2 hr Spring 2017 3/2/2018

Q1) Temperature sensor sensitivity is $4\Omega/^\circ\text{C}$, in the range ($\pm 25^\circ\text{C}$) and its value at 0°C is 280Ω . Using Wheatstone bridge convert its range to volt, and send its value using (4mA \sim 20mA transmitter), and prepare it for 8bit ADC with voltage reference (0-5Vref).
a) What is the digital output of ADC at the temperature -2°C . [12 pts]

Q2) Accelerometer sensor sensitivity is 0.33mA/g , used for measuring Acceleration in the range ($\pm 20\text{ g}$). Design signal condition circuits for bipolar (8 bit) ADC with voltage reference $\pm 4\text{V}$.

- a) What is the digital output of ADC at the acceleration is -3 g . [12]
- b) What is the acceleration when the digital output is 06H. [12 pts]

Q3) Design the signal conditioning circuits to connect the sensor to 10 bit ADC with voltage reference (0-5V), where: sensor output range ($-150 \sim +150\text{ mV}$) with frequency 15Hz. Noise signal 20mV with frequency 150Hz, and design filter that Attenuate the noise signal to 23%, and taking in account the effect of the filter on the sensor signal. [10 pts]

$V_s = 17.42\text{ mV}$

Q4) Using Thermocouple sensor (Type J) with 0°C reference, find the value of its output at 32°C . Design circuit to operate cooler if the temperature is more than 32°C , and using RTD with the following table using linear approximation of resistance versus temperature find the value of the RTD at 13°C and design circuit operate heater if the temperature is less than 13°C . [12 pts]

Temperature ($^\circ\text{C}$)	0	5	10	15	20
Resistance (Ω)	107.6	109.1	110.2	111.3	111.7

Q5) What is the sampling and sample and hold and aliasing and oversampling (Draw as you can) [4 pts]

Good Luck (Zeyad)

b) 0.184 find P $184 = 24$

$$V_o = (24 \times 0.184) = 4.416 \text{ V} \Rightarrow V_{in} = \frac{V_o - 0.184}{M} = 0.283125 \text{ V}$$

$$I = \frac{V_{in}}{R} = 1.8875 \text{ mA}$$

$$P = \frac{(1.8875 - 4)}{2.13} = 16.25 \text{ bar} \quad \#$$

Q4. DAC in (01010101) = 85, $D = \frac{2}{2^8} = \frac{1}{128}$

$$V_{o1} = \frac{85}{128} = 0.6640625 \text{ V}$$

$$V_{o2} = V_{o1} \times 2.7 = 1.79296875 \text{ V}$$

$$D_o \Rightarrow D = \frac{5}{256} = \frac{5}{256}, \quad D_o = \frac{V}{D} = 91.8 \cdot 91 + 1.611011$$

Q5 a)

b) RTD find Quadratic Approximation then find @ 11.4

$$107.6 = 110.2 (1 + \alpha_1 (0 - 10) + \alpha_2 (0 - 10)^2) \Rightarrow 1$$

$$111.7 = 110.2 (1 + \alpha_1 (20 - 10) + \alpha_2 (20 - 10)^2) \Rightarrow 2$$

$$\begin{aligned} -10 \alpha_1 + 100 \alpha_2 &= \frac{12}{551} \\ 10 \alpha_1 + 100 \alpha_2 &= \frac{19}{1102} \end{aligned}$$

$$\alpha_1 = \frac{41}{22040}$$

$$\alpha_2 = \frac{11}{220400}$$

$$R = 110.2 (1 + \alpha_1 (11.4 - 10) + \alpha_2 (11.4 - 10)^2) = 110.47622 \Omega$$

Q1.a) 1- Explain what is meant by active and passive sensor?

2- State the tasks of signal conditioning?

3- Using block diagram, describe a data acquisition system?

Q1.b) An instrument measures resistance from 0 to 1500Ω . What is the uncertainty in an indicated measurement of 397Ω if instrument has an accuracy of (a) $\pm 0.5\%$ of FS (b) $\pm 0.5\%$ of span? [12 pts]

Q2.a) A current balance bridge has $R_1=R_2=10K\Omega$, $R_3=1K\Omega$, $R_4=950\Omega$, $R_5=50\Omega$, $V_s=10V$, and a high-impedance null detector. Find the current required to null the bridge if R_3 changes by 1Ω ?


Q2.b) An air conditioning should come on when the sum of the temperature and humidity sensor voltages does above $1V$. A threshold circuit in the air conditioner requires $5V$ for turn-on. Design an interface circuit to connect the two sensors to the air conditioning unit?

[10 pts]

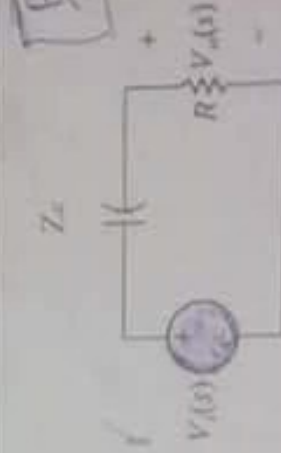Q3.a) For the following circuit:

1- Explain the behavior of the circuit when the frequency of the source changes from zero to infinity?

2- Derive the expressions of the transfer function and the cutoff frequency?



Q3.b) A displacement sensor has an input range of 0 to 3cm and a standard supply voltage $V_s=0.5V$. Using the calibration results in the table, estimate the sensitivity coefficients associated with supply voltage variations?

Input x (cm)	0	0.5	1	1.5	2	2.5	3
Output V (mV, $V_s=0.5$)	0	16.5	32	44	51.5	55.5	58
Output V (mV, $V_s=0.6$)	0	21	41.5	56	65	70.5	74

[10 pts]

Good Luck

$$\sqrt{(\omega B)^2 + \omega^2}$$

2664 32 16 8 4 2 1

University of Tripoli - Faculty of Engineering
Electrical & Electronic Engineering Department

EE463 Final Exam Time: 2 hr Spring 2017 3/2/2018

Q1) Temperature sensor sensitivity is $4\Omega/^\circ\text{C}$, in the range ($\pm 25^\circ\text{C}$) and its value at 0°C is 280Ω . Using Wheatstone bridge convert its range to volt, and send its value using 4mA $\sim 20\text{mA}$ transmitter, and prepare it for 8bit ADC with voltage reference $0.5V_{\text{ref}}$.
a) What is the digital output of ADC at the temperature -2°C . [12 pts]

Q2) Accelerometer sensor sensitivity is 0.33mA/g , used for measuring Acceleration in the range ($\pm 20\text{g}$). Design signal condition circuits for bipolar (8 bit) ADC with voltage reference $\pm 4V$.

- a) What is the digital output of ADC at the acceleration is -3g . [12]
b) What is the acceleration when the digital output is $06H$. [12 pts]

Q3) Design the signal conditioning circuits to connect the sensor to 10 bit ADC with voltage reference ($0-5V$), where: sensor output range ($-150 - +150\text{mV}$) with frequency 15Hz . Noise signal 20mV with frequency 150Hz , and design filter that Attenuate the noise signal to 2% , and taking in account the effect of the filter on the sensor signal. [10 pts]

$V_s = 1V$, $V_r = 17.42\text{mV}$

Q4) Using Thermocouple sensor (Type J) with 0°C reference, find the value of its output at 32°C . Design circuit to operate cooler if the temperature is more than 32°C , and using RTD with the following table using linear approximation of resistance versus temperature find the value of the RTD at 13°C and design circuit operate heater if the temperature is less than 13°C . [12 pts]

RTD: 110.2Ω
 $V_{in} = 1.476\text{mV}$

Temperature ($^\circ\text{C}$)	0	5	10	15	20
Resistance (Ω)	107.6	109.1	110.2	111.1	111.7

Q5) What is the sampling and sample and hold and aliasing and oversampling (Draw as you can). [4 pts]

Good Luck (Zeyad)

fall 2018

a. RTD Pt100 range (22 ~ 190)°C for 5°C (0 ~ 3)V

$V_s = 9V$, $R_1 = 200\Omega$. Sensitivity = $0.895mV/^\circ C$ @ $0^\circ C$

a) 22°C ~ 190°C

ohm range (100 + 22.039) = 108.588 ~ 100 + 190.039 = 174.102

$R_1 = 200\Omega$ $R_2 = 108.58\Omega$ assume $R_2 = 108.58\Omega$ or 174.1

$$R_3 = \frac{R_1 R_2}{R_1} = 200\Omega \text{ if Bridge}$$

المشغل طالب الهندسة

$$R_1 = 200\Omega \quad Q_{min} = 9 \times \frac{108.58}{200 + 108.58} = 3.16V$$

$$Q_{max} = 9 \times \frac{174.1}{200 + 174.1} = 4.1884V$$


Voltage range (3.16V ~ 4.1884V)

$$O = 3.16mV + offset \Rightarrow M = 2.936502289$$

$$3 = 4.1884mV + offset \quad offset = -9.299399725$$

$$V_0 = 2.936502289 \quad V_0 - 9.299399725$$
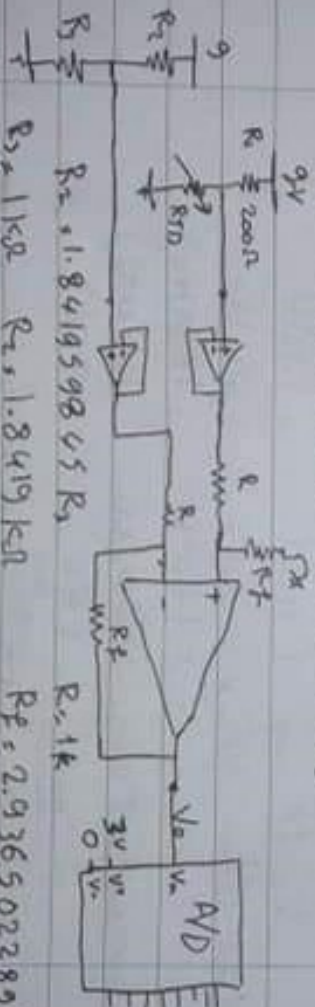
$$V_0 = 2.936502289 (V_{in} - 3.1668287)$$



$$b) (100 \times 0.39) + 100 = 139.5^\circ C \quad V_0 = 9 \times \frac{139}{200 + 139} = 3.650265482V$$

$$V_0 = 1.537073326V \Rightarrow D_0 = \frac{V_0}{2} = \frac{1.537073326}{2} = 0.768536663V$$

$$D_0 = 131.16 = 131 \quad 10000011$$



$$a) T_0 - 2^C \Rightarrow (-2 \times 4) + 280 + 272 \Omega$$

$$V_b \approx 9 \frac{2^{32}}{2^{32} + 180} = \frac{612}{113} V$$

$$V_{AB} = \frac{412}{113} - 4.5 = \frac{707}{113} V$$

$$V_{b1} = V_{AB} + 1 = \frac{612}{113} + 1$$

$$V_{b2} = (V_{b1} - 1) \frac{18}{113} = \frac{323}{113}$$

$$\Delta = \frac{5}{12} = \frac{5}{12}$$

$$P_{0.5} \frac{V_{b2}}{D} = 145.8923151 = 145.8923151$$

$$Q_{22}) 0.33 \text{ mA/g} \pm 20 \text{ g} \text{ b.i.f.l.w. } 8 \text{ bit} \pm 4 \text{ V}$$

$$-20 \times 0.33 = -6.6 \text{ mA} \approx 20 \times 0.33 = 6.6 \text{ mA}$$

$$\text{assume } R_{100\Omega} \Rightarrow -0.66 \text{ V} \approx 0.66 \text{ V}$$

$$-4 = -0.66 \text{ mA} + x \Rightarrow M, \frac{100}{100} V_0 = \frac{200}{100} V_{in}$$

$$4 = 0.66 \text{ mA} + x \Rightarrow M, \frac{100}{100} V_0 = \frac{200}{100} V_{in}$$



$$a) -3 \Rightarrow -0.99 \text{ mA} = -0.099 \text{ V} \Rightarrow -0.6 \text{ V}$$

$$D_{0.5} \frac{-0.6 + 4}{D} = 108.8 \approx 108.8 \approx (01101100)_2$$

$$b) V_0 = (6 \times D) - 4 = -3.8125 \Rightarrow \frac{32}{100} - \frac{200}{100} \Rightarrow \frac{1}{100} \Rightarrow -6.290625 \text{ mA}$$

$$-19.0625 \text{ g} \times$$


Also - range (-150mV ~ 150mV) 10 bit ADC (0~5) 1.15Hz

Noise 20mV @ 150Hz Design 5C for ADC filter attenuate 25% noise.

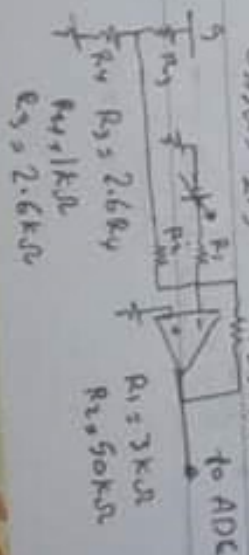b) Design

$$C_1 = -150 \text{ mV} + x \Rightarrow M, \frac{50}{100} V_{in} + 2.5$$

$$C_2 = 150 \text{ mV} + x \Rightarrow M, \frac{50}{100} V_{in} + 2.5$$



mintna

Superior Notepad

Sample
S.E.S.

University of Tripoli - Faculty of Engineering

Electrical & Electronic Engineering Department

EX463

Sample

Final Exam Time: 2 hr Spring 2018

17/7/2018

$$\frac{X}{K.A.s} = \frac{V}{K.A.s}$$

$$\frac{Sample}{Sub} = \frac{1}{K.A.s}$$

Q1) a- What is the meaning of single ended signal and differential signal.

b- Why sometimes we are holding the sampling signal.


Q2) Using Temperature sensor (sensitivity = 5mV/C), in the range (30C to 120C) and using voltage to frequency converter VFC (scale factor = 2V/1KHz). Calculate the sensor output range, and VFC output range. Using a counter to convert to digital with sampling rate 10sample/Sec, what is the value of the output of the counter if the temperature is 112C.

Q3) Barometer sensor sensitivity is 0.13mA/bar, used for measuring pressure in the range (± 20 bar) and the value of its output @ 0 bar is 4mA, using 150 Ω . Design signal condition circuits for bipolar (8 bit) ADC with voltage reference $\pm 4V$.

a) What is the digital output of ADC at the temperature is 8 bar.

b) What is the value of pressure when the digital output is 18H.

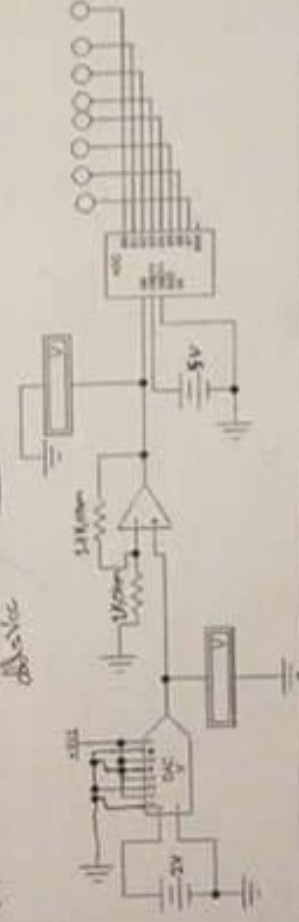Q4) What is the value of voltmeters and ADC output.



Q5) a- Using Thermocouple sensor Type J with 40C reference, What is the value of its output at the temperature 120C.

b- Using RTD with the following table using Quadratic approximation of resistance versus temperature find the value of the RTD at 11.4°C.


Temperature (°C)	0	5	10	15	20
Resistance (Ω)	107.8	109.1	110.2	111.1	111.7

Good Luck (Zeyad)

EE463

- Q1) What is the basic elements of a data acquisition system, explain two of them?
Q2) What is the difference between single ended signal and differential signal?
Q3) A length meter range is (0 ~ 5.5m) has quoted inaccuracy of $\pm 2\%$ F.S., what is the maximum measurement error expected for this instrument in centimeter.

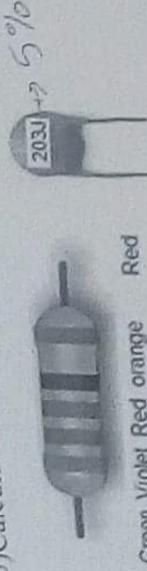- Q4) What is Zero drift and sensitivity drift?
Q5) Calculate the value of the following components:



Green Violet Red orange Red

- Q6) RTD with sensitivity $3\Omega/^\circ\text{C}$, and its value = 320Ω @ 0°C , use wheatstone bridge to calculate its range in volt for temperature range (0 ~ 70°C) . design s.c. circuit for ADC which voltage reference (0 ~ 4V) .



-Get the temperature equation

- Q7) sensitivity of pressure sensor is (2.8 mA/bar) working in the range (0~15bar), in a noisy area, design a circuit to transmit its data using (4m ~ 20mA) transmitter, What is the new range in volt of the sensor .

Good Luck

Better 3
Be 8
Right 7
or 6
your 5
Best 4
guess 3
goes 2
Very 1
Wrong 0

$A, B \times 10^c$

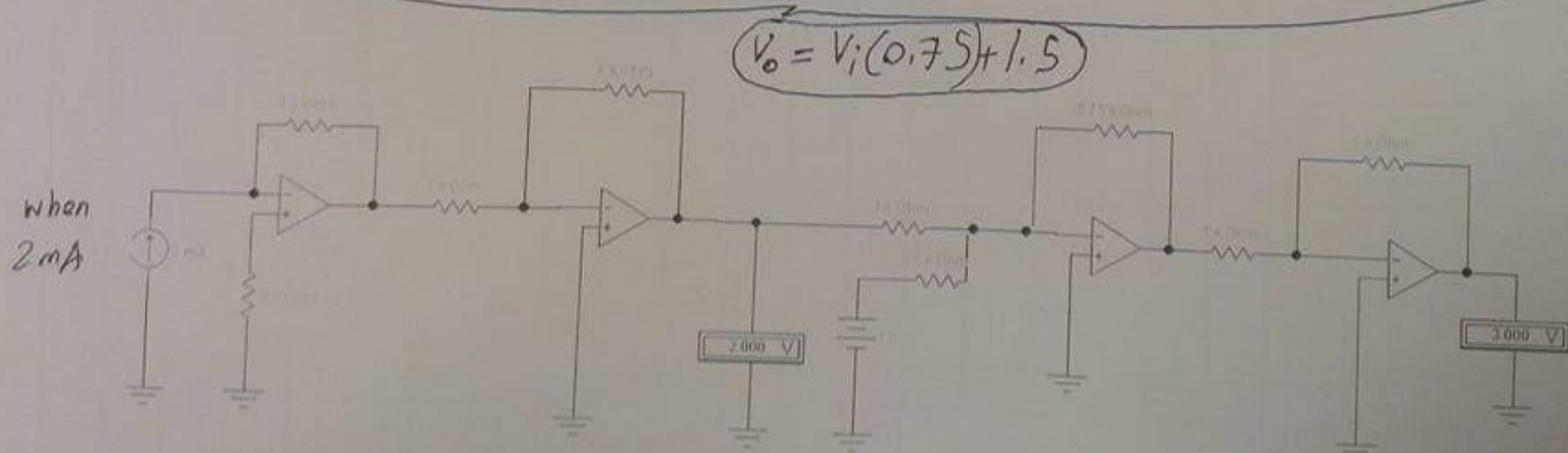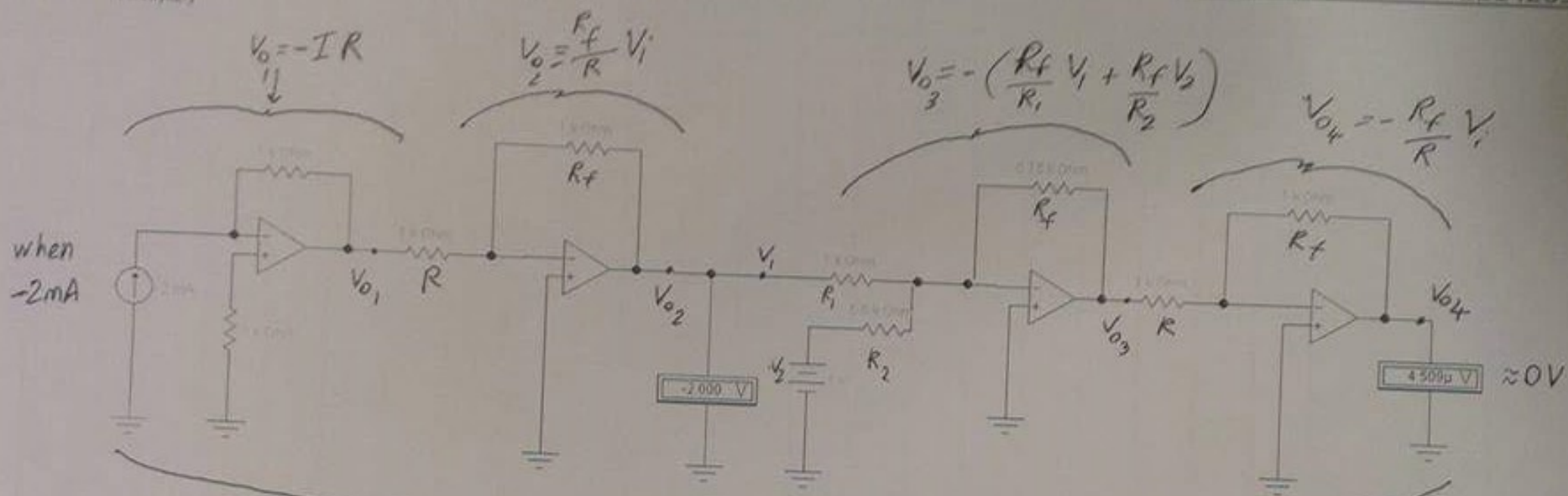

Q₁) Accelerometer sensitivity 0.2 mA/g
calculate its output range in

(+log), Design signal conditioning

circuit for (0~3V) ADC

range (2~2mA)
(0.2x-10 ~ 0.2x10 mA)
(-2 ~ 2V) , ideal all

(1K) 90910011

$$0 = -2M + \text{offset}$$

$$3 = 2M + \text{offset}$$

$$3 = 4M$$

$$M = \frac{3}{4}$$

$$V_o = V_i M + \text{offset}$$
$$= V_i (0.75) + 1.5$$

V_i	-2V	0	2V
V_o	0	1.5	3

Q2] Sensitivity $0.1V/g$ rang (0~8g) m/s^2
 we want to signal
 Condition data for converter to
 use it for (0~5) ADC

$$0 = 1M + offset$$


$$5 = 1.8M + offset$$

$$5 = 0.8M \Rightarrow M = \frac{5}{0.8} = 6.25$$

$$offset = -6.25$$

$$V_o = V_i \cdot 6.25 - 6.25 = 6.25(V_i - 1)$$

V_i	1	1.4	1.8
V_o	0	2.5	5

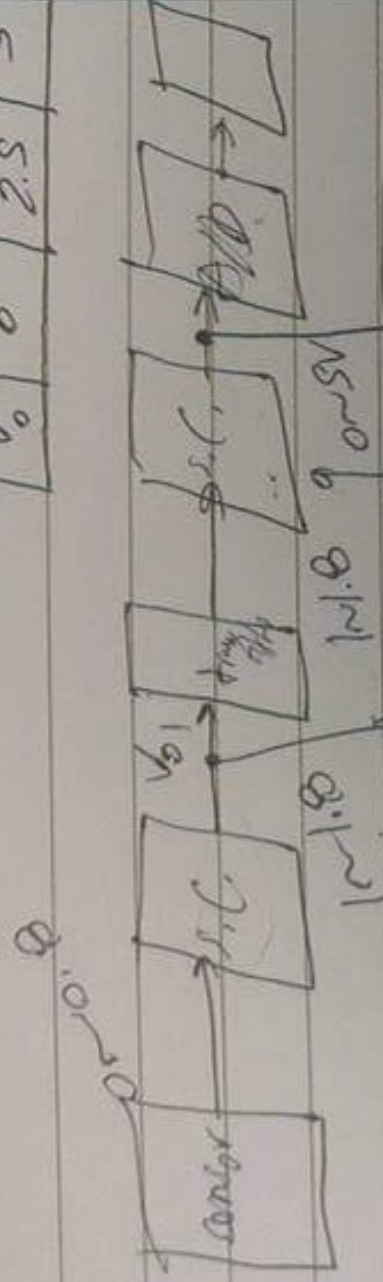

$$V_o = 1.8V + offset$$

$$5 = 1.8V + offset$$

$$V_{o2} = 6.25(V_i - 1)$$

$$V_{o1} = V_i + 1$$

Q4) Temperature sensor sensitivity is $452\text{ }^{\circ}\text{C}$, in the range (-25°C) and its value at 0°C is 280Ω . Using Wheatstone bridge convert its range to volt, and send its value using 4mA -20mA transmitter, and prepare it for 8bit ADC with voltage reference $0.5V_{\text{ref}}$.
a) What is the digital output of ADC at the temperature -2°C . [12 pts]

Q2) Accelerometer sensor sensitivity is 0.33mA/g , used for measuring Acceleration in the range (-20 g) . Design signal condition circuits for bipolar (8 bit) ADC with voltage reference $\pm 4\text{V}$.

- a) What is the digital output of ADC at the acceleration is -3 g .
b) What is the acceleration when the digital output is 06H. [12 pts]

Q3) Design the signal conditioning circuits to connect the sensor to 10 bit ADC with voltage reference (0.5V) , where sensor output range $(-150 - +150\text{ mV})$ with frequency 15Hz . Noise signal 20mV with frequency 150Hz , and design filter that Attenuate the noise signal to 25% , and taking in account the effect of the filter on the sensor signal. [10 pts]

Q4) Using Thermocouple sensor Type J with 0°C reference, find the value of its output at 32°C . Design circuit to operate cooler if the temperature is more than 32°C , and using RTD with the following table using linear approximation of resistance versus temperature, find the value of the RTD at 13°C and design circuit operate heater if the temperature is less than 13°C . [12 pts]

Temperature ($^{\circ}\text{C}$)	R	δ	θ	α	β
Resistance (Ω)	107.8	109.1	110.2	111.1	111.7

Q5) What is the sampling and sample and hold and aliasing and oversampling (Draw as you can) [4 pts]

Good Luck (Zcyad)

Q1) Temperature sensor sensitivity is $0.42\text{mA}/^{\circ}\text{C}$, used for temperature range $(\pm 50^{\circ}\text{C})$. Design signal condition circuits for bipolar (8 bit) ADC with voltage reference $\pm 3\text{V}$.


a) What is the digital output of ADC at the temperature 31°C , -20°C .

b) What is the temperature when the digital output is B6H. [10 pts]

Q2) Design the signal conditioning circuits to connect the sensor to 8 bit ADC with voltage reference $(0-10\text{V})$, where: sensor output range $(-100 \sim +100\text{ mV})$ with frequency 25Hz , Noise signal 20mV with frequency 260Hz , and using filter that Attenuate the noise signal to 29% of its value, and taking in account the effect of the filter on the sensor signal. [10 pts]

Q3) Using pressure sensor which sensitivity is $2.3\text{mV}/\text{bar}$, and temperature sensor which sensitivity is $10\text{mV}/^{\circ}\text{C}$ and its value at zero $^{\circ}\text{C}$ $\approx 300\Omega$. Design circuit which open Valve when the pressure is more than 15bar , and operate heater when temperature is less than 20°C , and operate Red LED when both of them are ON. [10 pts]

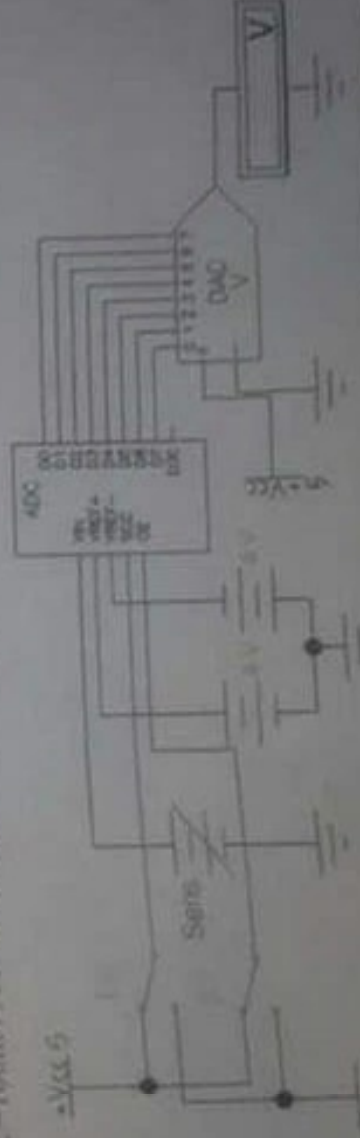Q4) What is the digital value of the ADC output and what is the analog value of DAC output at the temperature 23°C , and -30°C . Where: sensor sensitivity $= [5\text{mV}/^{\circ}\text{C}]$, sensor output at $0^{\circ}\text{C} = 100\text{mV}$, sensor range $= \pm 50^{\circ}\text{C}$. [10 pts]



- Q1) a-Using RTD PT100 for temperature range (22°C to 190°C), design a signal conditioning circuit for (0-3V) ADC. (use voltage divider circuit, $V_s=9V$, $R_1=200\Omega$).
b-If we will send the sensor output for a distance with same voltage reference.
c-What is the ADC digital output if the temperature is 100°C.
d-What is the temperature if the ADC output is (10011110).

$$V_{ref} = 2V \quad [14 \text{ pts}]$$

- Q2) Using Acceleration sensor (sensitivity = 0.14 mV/g), with offset $7 \text{ mA}@0g$, for the range ($\pm 30g$) and using voltage to frequency converter VFC (scale factor = $4V/6 \text{ KHz}$).
a-Draw the block diagram of the operation.

- b-Calculate the sensor output range, and VFC output range, digital output of counter if the sampling is each 0.2Sec.

- c-What is the value of the output of the counter if the acceleration is $0.5g$. [10 pts]

- Q3) Barometer sensor sensitivity is 5 mV/bar , and $5\Omega/\text{cm}$ pot. level sensor for 150cm range used for measuring level ($V_s=9V$ use, $R_1=150\Omega$). Design circuit to turn ON green LED if (level more than 70cm and pressure less than 5bar), red LED if one of them opposite these values. [10 pts]

- Q4) What is the value of voltmeters and ADC and DAC outputs. [8 pts]



- Q5) a- Using Thermocouple sensor Type K with 0°C reference, What is the value of temperature if its output is 19 mV . What is its output at the temperature $V_{out}(-40^\circ\text{C})=?$. (8pts)

EE463

University of Tripoli - Faculty of Engineering
Electrical & Electronic Engineering Department

Final Exam

Time: 2 hr

Spring 2017

5/2/2018

Q1) Temperature sensor sensitivity is $40 \mu\text{V}/^\circ\text{C}$, in the range $(\pm 25^\circ\text{C})$ and its value at 0°C is 280mV . Using Wheatstone bridge convert its range to volt, and send its value using (4mA $\pm 20\text{mA}$ transmitter) and prepare it for 8bit ADC with voltage reference (0-5V)ref.

a) What is the digital output of ADC at the temperature -2°C . [12 pts]

Q2) Accelerometer sensor sensitivity is 0.33mA/g , used for measuring Acceleration in the range $(\pm 20\text{g})$. Design signal condition circuits for bipolar (8 bit) ADC with voltage reference $\pm 4\text{V}$.

a) What is the digital output of ADC at the acceleration is -3g . [12

b) What is the acceleration when the digital output is 06H. -19 [12 pts]

Q3) Design the signal conditioning circuitry to connect the sensor to 10 bit ADC with voltage reference (0-5V), where: sensor output range $(-150 \sim +150\text{mV})$ with frequency 15Hz, Noise signal 20mV with frequency 150Hz, and design filter that Attenuate the noise signal to 25%, and taking in account the effect of the filter on the sensor signal.

$$V_f = V_i \sqrt{2} \times 0.25 \times 0.75$$

Q4) Using Thermocouple sensor Type J with 0°C reference, find the value of its output at 32°C . Design circuit to operate cooler if the temperature is more than 32°C , and using RTD with the following table using linear approximation of resistance versus temperature find the value of the RTD at 13°C and design circuit operate heater if the temperature is less than 13°C .

Temperature ($^\circ\text{C}$)	6	5	16	15	20
Resistance (Ω)	107.6	109.1	110.2	111.1	111.7

Q5) What is the sampling and sample and hold and aliasing and oversampling (Draw as you can) [4 pts]

Good Luck (Zeyad)

- Q1) a-What is the meaning of single ended signal, differential signal and give example.
b- What is sample and what is hold and when we use them. [6 pts]

Q2) Using Temperature sensor (RTD-PT100), in the range (30C to 90C) and using Wheatstone bridge ($V_s=9V$, $R1=110$, $R2=120$), and using voltage to frequency converter VFC (scale factor = $10KHz/1.12V$).

- a- Calculate the sensor output range, Wheatstone bridge output range and VFC output range.
b- Using a counter to convert to digital with sampling rate 180 sample/Sec, What is the output range of the counter, what is the value of the output of the counter if the temperature is $40C$. 552
c- Draw Block diagram of the circuit. [16 pts]

Q3) An accelerometer sensor sensitivity is $0.145mV/g$, used for measuring pressure in the range ($\pm 20 g$), and the value of its output @ $0 g$ is $5.2mA$, using 190Ω converting to volt resistance, Design signal condition circuits for bipolar (8 bit) ADC with voltage reference $\pm 4V$.

- a) Calculate sensor output range (current, voltage, Binary).
b) What is the digital output of ADC at the acceleration is $8 g$.
c) What is the value of acceleration when the digital output is $0DH.92H$. [15 pts]
d) If the frequency of the signal is $120Hz$ and there is unwanted noise with frequency $15KHz$, design filter that attenuate the noise to 18% of its value, calculate the effect on the sensor output range. [05 pts]

Q4) Using RTD with the following table using Quadratic approximation of resistance versus temperature find the value of the RTD at $12.4^{\circ}C$.

Temperature ($^{\circ}C$)	0	5	10	15	20
Resistance (Ω)	103.6	105.1	106.3	107.1	108.3

[08 pts]

Q1.a) An alarm light goes ON when a pressure sensor voltage rises above 4.00 V. The pressure sensor outputs 20 mV/kPa and has a time constant of 4.9 s. How long after the pressure rises suddenly from 100 kPa to 400 kPa does the light go ON?

Q1.b) A load cell is calibrated at $21\epsilon^a$ and has the following deflection/load characteristic:

Load(kg)	0	50	100	150	200
Deflection (mm)	0	1	2	3	4

When used at $35\epsilon^a$, its characteristic changes to the following:

Load(kg)	0	50	100	150	200
Deflection (mm)	0.2	1.3	2.4	3.5	4.6

Determine the sensitivity coefficients

[10 pts]

Q2.a) A measurement signal has a frequency less than 1KHz, but there is unwanted noise at about 1MHz. Design a filter that attenuate the noise to 1% using a capacitor $0.01\mu\text{f}$. What is the effect on the measurement signal at its maximum of 1KHz (give a comment on the result)?

Q2.b) Signal conditioning analysis shows that the following equation must relate output voltage to input voltage: $V_o = 3.35V_{in} - 2.68$. Design circuits to do this using a differential amplifier? [12 pts]

Q3.a) Using timing diagram, explain the control lines that coordinate the operation of ADCs?

Q3.b) Design a 5-bit weighted-resistor DAC whose full-scale output voltage is -15v. Logic levels are 1=5v and 0=0v. What is the output voltage when the input is 01010?

[10 pts]

$$T = \frac{R}{R_0} \left(\frac{1}{\alpha} + \frac{1}{\beta} \right)$$

Q1) a- Using RTD PT100 for temperature range (22°C to 190°C), design a signal conditioning circuit for (0-3V) ADC. (use voltage divider circuit, $V_S = 9V$, $R1 = 200\Omega$).

~~b- If we will send the sensor output for a distance with same voltage reference.~~

c- What is the ADC digital output if the temperature is 100°C.

d- What is the temperature if the ADC output is (10011110).

[14 pts]

Q2) Using Acceleration sensor (sensitivity -0.14mV/g), with offset $7\text{mA}@0\text{g}$, for the range ($\pm 30\text{g}$) and using voltage to frequency converter VFC (scale factor $= 4\text{V}/6\text{KHz}$).

a- Draw the block diagram of the operation.

b- Calculate the sensor output range, and VFC output range, digital output of counter if the sampling is each 0.2Sec.

c- What is the value of the output of the counter if the acceleration is -0.5g .


[10 pts]

Q3) Barometer sensor sensitivity is 5mV/bar , and $5\Omega/\text{cm}$ pot. level sensor for 150cm range used for measuring level ($V_S = 9V$ use, $R1 = 150\Omega$). Design circuit to turn ON green LED if (level more than 70cm) and pressure less than 5bar), red LED if one of them opposite these values.

[10 pts]

Q4) What is the value of voltmeters and ADC and DAC outputs

[8 pts]

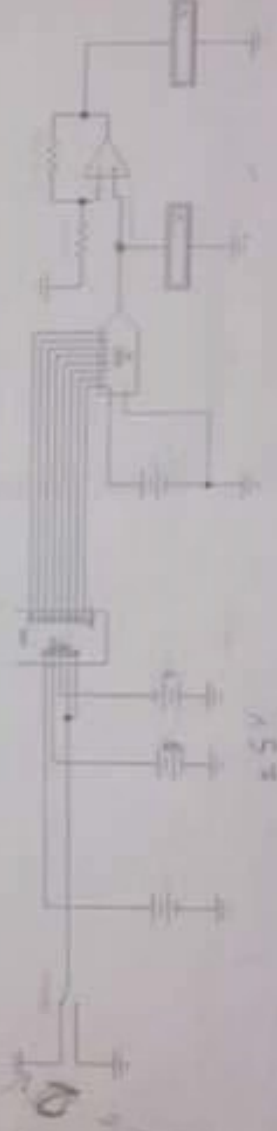

Q5) a- Using Thermocouple sensor Type K with 0°C reference, What is the value of temperature if its output is 19mV, What is its output at the temperature $V_{K10}(-40^\circ\text{C}) = 2$.


[8pts]

- Q1) What is the basic elements of a data acquisition system, explain two of them?
Q2) What is the difference between single ended signal and differential signal?
Q3) A length meter range is (0 ~ 5.5m) has quoted inaccuracy of $\pm 2\%$ F.S., what is the maximum measurement error expected for this instrument in centimeter.

Q4) What is Zero drift and sensitivity drift?

$$\begin{aligned} 100\% &= 5.5 \text{ m} = 550 \text{ cm} \\ 100000\% &= 55000 \text{ cm} = 550 \text{ m} \\ 100 - \text{red} &= 2 \\ 1000 - \text{orange} &= 3 \end{aligned}$$

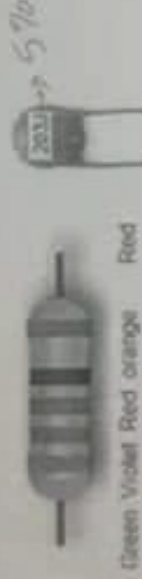Q5) Calculate the value of the following components:



Green Violet Red orange Red

Q6) RTD with sensitivity $3\Omega/^\circ\text{C}$, and its value = 320Ω @ 0°C , use wheatstone bridge to calculate its range in volt for temperature range (0 ~ 70°C), design s.c. circuit for ADC which voltage reference (0 ~ 4V).

-Get the temperature equation

Q7) sensitivity of pressure sensor is (2.8 mA/bar) working in the range (0 ~ 15bar), in a noisy area, design a circuit to transmit its data using (4m ~ 20mA) transmitter, What is the new range in volt of the sensor.

Good Luck

Better 3
Be 3
Right 7
or 6
your 5
Best 4
guess 3
goes 2
Very 1
Wrong 0

A. B $\times 10^2$